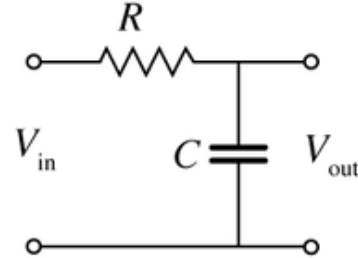


### Homework 3

At time  $t = 0$  the potential difference  $V_{in}$  switches suddenly from 0 to  $V_0$ . Calculate  $V_{out}$  as a function of time for  $t > 0$  and sketch  $V_{out}(t)$ .




---

**Solution:** The voltage out is equal to the voltage over the capacitor. We know that the voltage over the capacitor is  $\frac{Q}{C}$  where  $Q$  is the charge on the capacitor and  $C$  is the capacitance of the capacitor. We start with

$$\begin{aligned}\frac{dV_C}{dt} &= \frac{1}{C} \frac{dQ}{dt} \\ &= \frac{I}{C}\end{aligned}$$


We know that  $I = \frac{V_{in} - V_C}{R}$ , so

$$\begin{aligned}\frac{dV_C}{dt} &= \frac{V_{in} - V_C}{RC} \\ \frac{dV_C}{V_{in} - V_C} &= \frac{dt}{RC} \\ \int \frac{dV_C}{V_{in} - V_C} &= \int \frac{dt}{RC} \\ -\ln(V_{in} - V_C) &= \frac{t}{RC} + C \\ V_{in} - V_C &= Ae^{-t/RC} \\ V_C &= V_{in} - Ae^{-t/RC}\end{aligned}$$

We know that initially,  $V_C$  is zero, so our final equation for  $V_{out}$  is (since  $V_C = V_{out}$  and  $V_{in} = V_0$ ):

$$V_{out} = V_0 \left(1 - e^{-t/RC}\right)$$

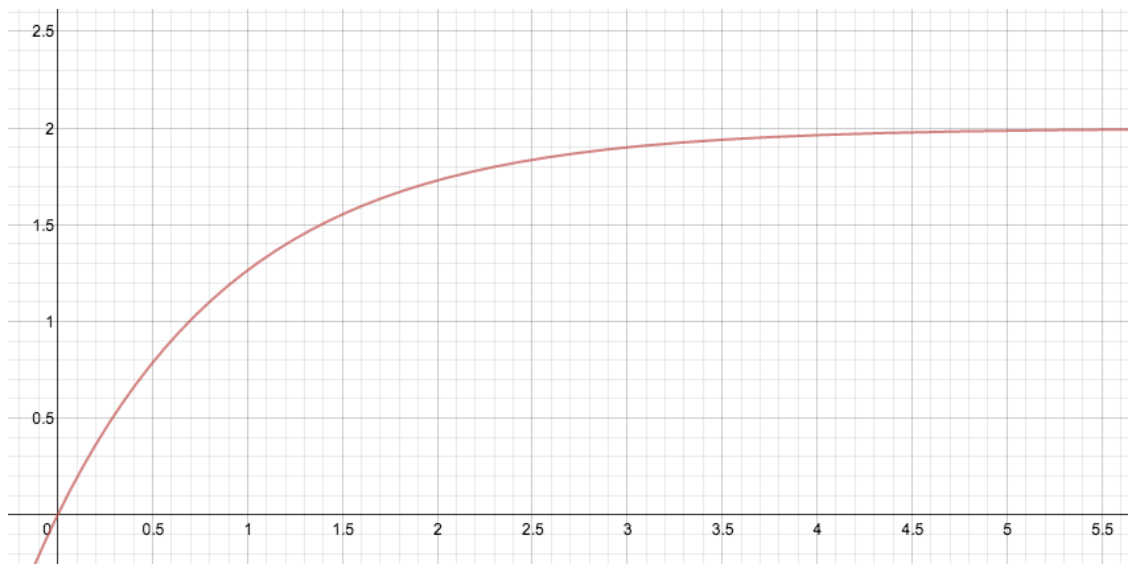A graph of this function yields the following result.



Notice that the voltage starts at zero, then exponentially approaches  $V_{in}$ , which was 2 V in this case. ■

---