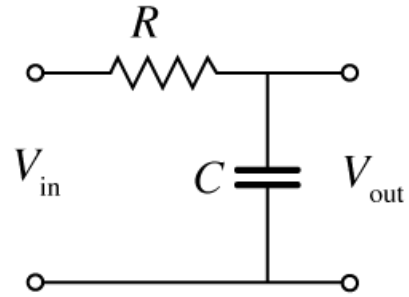


At time $t=0$ the potential difference V_{in} switches suddenly from 0 to V_0 . Calculate V_{out} as a function of time for $t > 0$ and sketch $V_{out}(t)$.

Hints

1. See the top of *this page* for the relationship between charge Q and voltage across a capacitor, and between current $I = dQ/dt$ and voltage across a resistor.
2. See *this page* for a discussion of the method of separation of variables.



So after being confused by the unfamiliar notation for a bit and asking Tasha for clarification, I redrew this as a simple RC circuit in the form I know and love, with a voltmeter hooked up to measure the voltage difference around the capacitor. I already analyzed this for the capacitor lab, but I might as well recopy the work here. First I find an equation for the charge as a function of time.

$$\Delta V_{throughCircuit} = 0$$

$$V_0 - V_{capacitor} - V_{resistor} = 0$$

$$V_0 - \frac{q}{C} - \frac{dq}{dt}R = 0$$

$$V_0 - \frac{q}{C} = \frac{dq}{dt}R$$

$$V_0C - q = \frac{dq}{dt}RC$$

$$\frac{1}{RC} = \frac{1}{V_0C - q} \frac{dq}{dt}$$

$$\int_0^t \frac{1}{RC} dt = \int_0^q \frac{1}{V_0C - q} dq$$

$$\frac{t}{RC} = -\ln(V_0C - q)_0^q$$

$$-\frac{t}{RC} = \ln(V_0C - q) - \ln(V_0C) = \ln\left(\frac{V_0C - q}{V_0C}\right)$$

$$e^{-\frac{t}{RC}} = \frac{V_0C - q}{V_0C} = 1 - \frac{q}{V_0C}$$

$$1 - e^{-\frac{t}{RC}} = \frac{q}{V_0C}$$

$$V_0C(1 - e^{-\frac{t}{RC}}) = q$$


With this expression for charge as a function of time, we know that the voltage across the capacitor is the ratio of charge and its capacitance, so we can get V_C :

$$C = \frac{q}{V_C} = \frac{V_0 C (1 - e^{-\frac{t}{RC}})}{V_C}$$

$$1 = \frac{V_0 (1 - e^{-\frac{t}{RC}})}{V_C}$$

$$V_C = V_0 (1 - e^{-\frac{t}{RC}})$$

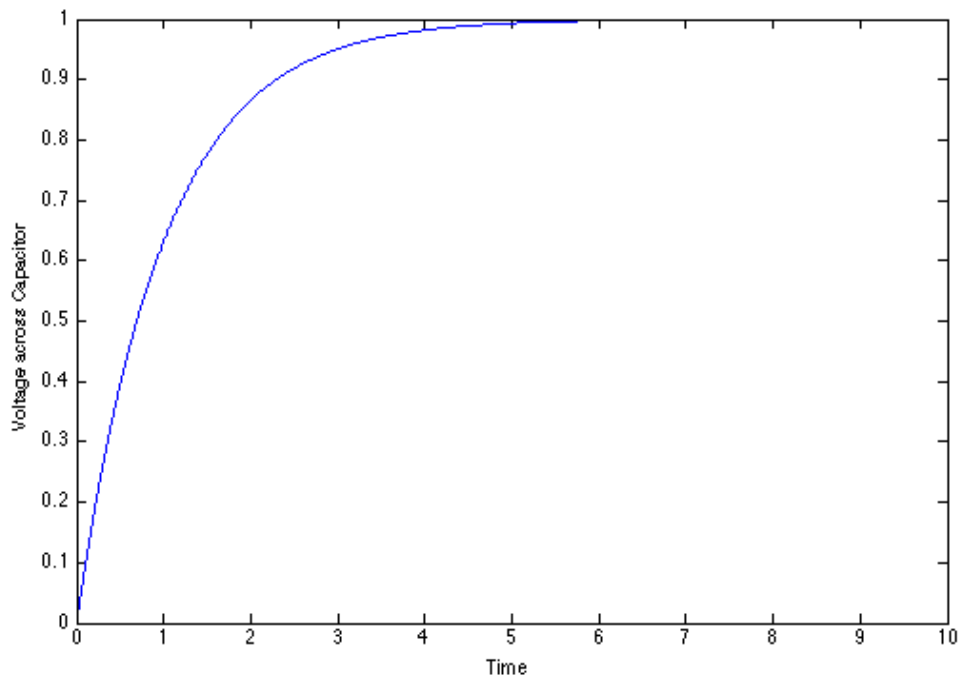Here's a sketch for V_C with V_0 , R and C all 1. $V_C = 1 - e^{-t}$



■