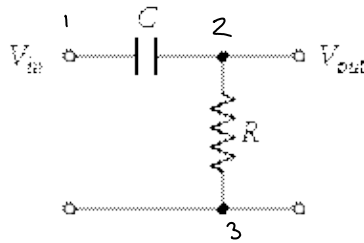


HW3

12 October 2013

13:13



We know that

$$V_C = \frac{Q}{C} \text{ for capacitors,}$$

$$V_R = IR \text{ for resistors,}$$

and Kirchhoff's current

law says $I_{12} + I_{23} = 0$, given an open circuit as

$$V_{out} - V_{in} = \int I_{12} / C \quad \text{and} \quad V_{out} - V_{in} = I_{23} R$$

$$\dot{Q}(V_{out} - V_{in}) \cdot C = I_{12} \quad I_{23} = -\frac{1}{R} (V_{out} - V_{in})$$

$$C(\dot{V}_{out} - \dot{V}_{in}) - \frac{1}{R} (V_{out} - V_{in}) = 0$$

$$\dot{V}_{out} - \dot{V}_{in} - \frac{1}{RC} (V_{out} - V_{in}) = 0$$

$$V_{out} = V_0 e^{-\frac{1}{RC} t}$$

